

Design of All Digital FM Receiver Circuit



Nursani Rahmatullah
March 2005

Table of Contents

| | |
|--|----|
| Table of Contents | i |
| Table of Figures | ii |
| 1. Introduction..... | 1 |
| 2. Architecture Description..... | 1 |
| 2.1 Phase Detector | 1 |
| 2.2 Loop Filter | 3 |
| 2.3 Numerical Controlled Oscillator..... | 4 |
| 2.4 FIR Filter..... | 6 |
| 3. Functional Explanation | 6 |
| 4. Critical Path Speed and Circuit Area..... | 9 |
| 5. Appealing Point and Originality | 11 |
| 6. HDL Codes | 11 |
| 6.1 Multiplier (Phase Detector)..... | 11 |
| 6.2 Loop Filter | 13 |
| 6.3 Numerical Controlled Oscillator (NCO)..... | 14 |
| 6.4 FIR Filter..... | 18 |
| 6.5 Circuit (top level design) | 19 |
| 6.6 Test Bench | 20 |
| 7. Simulation Waveform..... | 21 |
| 8. FPGA Implementation..... | 22 |
| 9. Closing | 25 |
| Reference: | 25 |
| Appendix:..... | 26 |

Table of Figures

| | |
|--|----|
| Fig. 1 Block diagram of All Digital FM Receiver circuit..... | 1 |
| Fig. 2 Block diagram of multiplier as phase detector | 2 |
| Fig. 3 Paper and pencil illustration of Booth's algorithm..... | 3 |
| Fig. 4 Block diagram of first order loop filter | 4 |
| Fig. 5 Block diagram of NCO..... | 5 |
| Fig. 6 Data values in one cycle of cosine ROM | 5 |
| Fig. 7 Block diagram of FIR filter | 6 |
| Fig. 8 Complete block diagram of All Digital FM Receiver system..... | 7 |
| Fig. 9 Block diagram of PLL system in analyzing transient response..... | 8 |
| Fig. 10 Unit step response for PLL system used in FM receiver system..... | 9 |
| Fig. 11 Simulation waveform of the circuit, subjected to square wave modulated input signal..... | 22 |
| Fig. 12 Simulation waveform of the circuit, subjected to triangular wave modulated input signal..... | 22 |
| Fig. 13 Chip graphic for the design | 23 |
| Fig. 14 Capturing output data via parallel cable in JTAG mode | 23 |
| Fig. 15 Captured data and waveform of the output in ChipScope..... | 24 |
| Fig. 16 Actual demodulated data | 24 |

1. Introduction


The design of the All Digital FM Receiver circuit in this project uses Phase Locked Loop (PLL) as the main core. The task of the PLL is to maintain coherence between the input (modulated) signal frequency, ω_i and the respective output frequency, ω_o via phase comparison. This self-correcting ability of the system also allows the PLL to track the frequency changes of the input signal once it is locked.

Frequency modulated input signal is assumed as a series of numerical values (digital signal) via 8-bit of analog to digital conversion (ADC) circuit. The FM Receiver gets the 8 bit signal every clock cycle and outputs the demodulated signal.

The All Digital FM Receiver circuit is designed using VHDL, then simulated and synthesized using ModelSim SE 6 simulator and Xilinx ISE 6.3i, respectively. FPGA implementation also provided, here we use Virtex2 device. The real measurement is done using ChipScope Pro 6.3i.

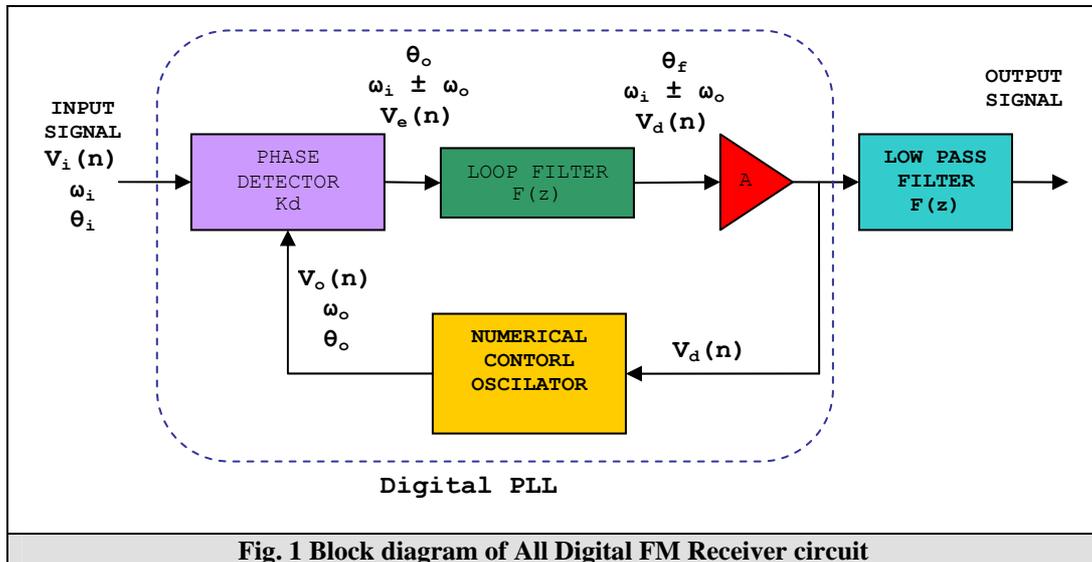2. Architecture Description

The system of All Digital FM Receiver consists of a digital PLL cascaded with digital low pass filter. The block diagram of system is shown in Fig. 1.



2.1 Phase Detector

Phase Detector (PD) detects phase error between input signal and output signal from NCO. This operation employs a multiplier module. The input signal is frequency modulated, so the input signal $V_i(n)$ can be expressed as follows,

$$V_i(n) = \sin(\omega_i n + \theta_i) \quad (1)$$

Feedback loop mechanism of the PLL will force NCO to generate sinusoidal signal $V_o(n)$ with the same frequency of $V_i(n)$, then


$$V_o(n) = \cos(\omega_o n + \theta_o) \quad (2)$$

Output of phase detector is product of these two signals, using familiar trigonometric identity we obtain

$$\begin{aligned} V_d(n) &= K_d \sin(\omega_i n + \theta_i) \cos(\omega_o n + \theta_o) \\ &= \frac{K_d}{2} [\sin(2\omega_i n + \theta_i + \theta_o) + \sin(\theta_i - \theta_o)] \end{aligned} \quad (3)$$

K_d is the gain of the phase detector. The first term in (3) corresponds to high frequency component. The second term corresponds to the phase difference between $V_i(n)$ and $V_o(n)$. By removing the first term thru loop filtering, the phase difference can be obtained.

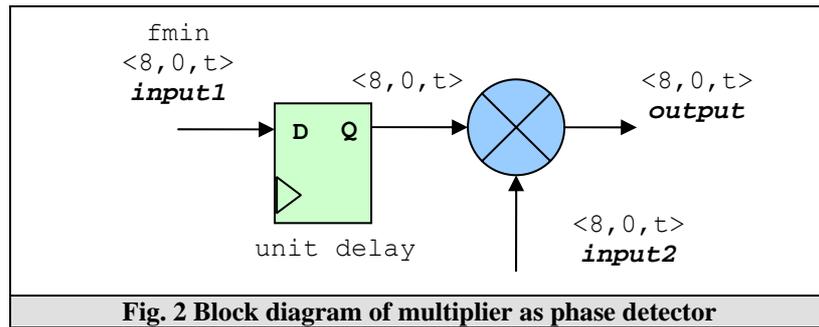The block diagram of phase detector is a multiplier shown in Fig. 2.




Summary of operation:

- *input1* is *fmin* (modulated data), *input2* is NCO's output. Both input are 2's complement in $\langle 8, 0, t \rangle$ format, please see [8] for details.
- unit delay is used to synchronize operation,
- then inputs values are multiplied, where *input1* as multiplicand and *input2* as multiplier,
- product will be 16 bit in $\langle 16, 0, t \rangle$ format, then we scale it by cropping the 8 most bits and feed it to the output in $\langle 8, 0, t \rangle$ format.

In the VHDL model, we use *Booth's Multiplication algorithm* [2] instead of simple signed arithmetic multiplier operation (denoted by $*$). Arithmetic multiplier will consume large area, while Booth's multiplication algorithm for 8-bit multiplication only needs eight 8-bit adders which is much save in area consumption.

For this algorithm, as shown in Fig. 3, the individual partial products determined from the multiplicand may be: added to, subtracted to, or may not change the final product at all based on the following rules:

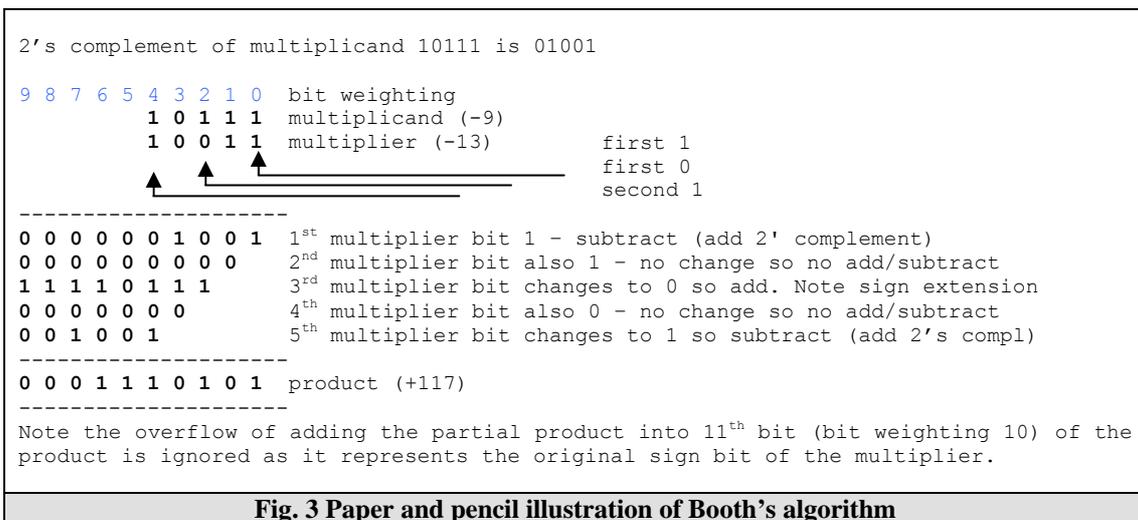- the multiplicand is subtracted from the partial product upon encountering the first 1 in a string of 1's in the multiplier,
- the multiplicand is added to the partial product upon encountering the first 0 provided that there was no previous 1 in a string of 0's in the multiplier,
- the partial product does not change when the bit is identical to the previous multiplier bit.



2.2 Loop Filter

Loop filter will remove the high frequency component in (3). Fig. 4 shows the block diagram of a first order loop filter used in the receiver system. In the VHDL model of this block, we need to treat a sign extension from $\langle 8, 0, t \rangle$ to $\langle 12, 4, t \rangle$ and a multiplication by constant of 15/16.


Summary of operation:

- input C is multiplier's output in $\langle 8, 0, t \rangle$ format. Output is $DI \langle 12, 4, t \rangle$. DI will be multiplied by 15/16 and then the product is summed back to C
- $dtemp \langle 12, 4, t \rangle$ is internal signal which is the summing result of C and DI . C must be changed to $\langle 12, 4, t \rangle$ before summation, hence,

| | $\langle 8, 0, t \rangle$ | $\langle 12, 4, t \rangle$ |
|-----|---------------------------|--|
| C | $C(7 \text{ downto } 0)$ | $C(7) \& C(7) \& C(7) \& C(7) \& C(7 \text{ downto } 0)$ |

- $dtemp$ will be assigned to $D1$. Then $dtemp \times 15/16 = dtemp \times (1 - 1/16) = dtemp - E$
- $E = dtemp \times 1/16$, in reality $1/16$ multiply can be implemented by just 4 bit right shift operation. Then no multiplier is required.

| | |
|----------------------------------|---|
| $dtemp \langle 12, 4, t \rangle$ | $E \langle 12, 4, t \rangle = dtemp \times 1/16$ |
| $dtemp(11 \text{ downto } 0)$ | $dtemp(11) \& dtemp(11) \& dtemp(11) \& dtemp(11) \& dtemp(11 \text{ downto } 4)$ |

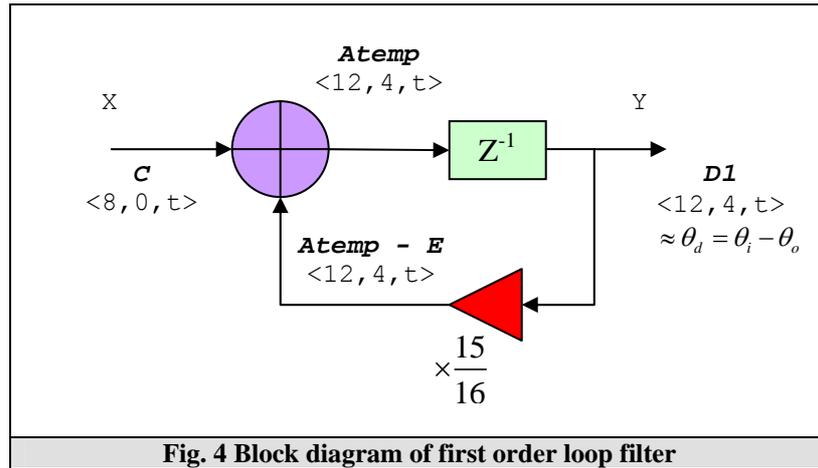


First order loop filter as shown in Fig. 4 is a low pass filter with the transfer function

$$H(z) \equiv \frac{Y(z)}{X(z)} = \left(\frac{1}{z - 0.9375} \right) \quad (4)$$


Which has a pole on the real axis at $z = 0.9375$. From stability property of discrete time filter, we know that $H(z)$ is stable since its pole is located within the unit circle [1].

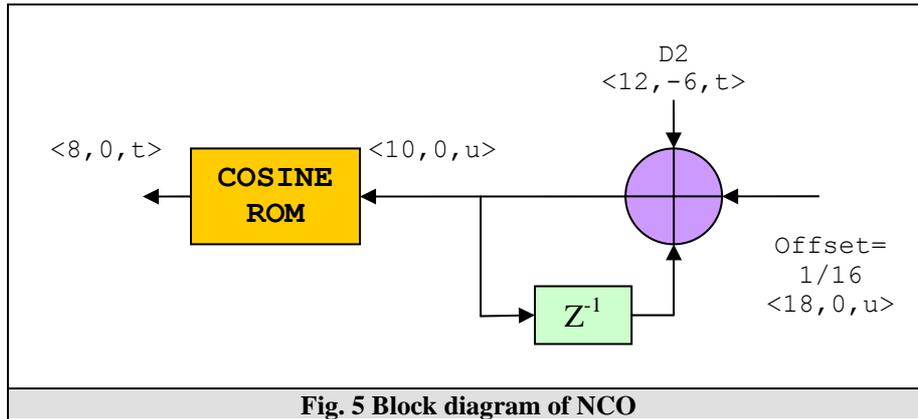2.3 Numerical Controlled Oscillator

Numerical Controlled Oscillator (NCO) will take the corrective error voltage, $V_d(n)$ and then shift its output frequency from its free-running value to the input signal frequency ω_i and thus keep the PLL in lock. The block diagram can be seen in Fig. 5 as follows,



Here we assume the NCO free running frequency is 1 MHz and the system clock frequency is 16 MHz; there are 16 sampling points in one cycle of 1 MHz free running frequency. When input is zero, NCO has to generate output equal to free running frequency. Since there are 16 sampling points in one cycle of free running frequency, so the offset must be 1/16. The greater input will produce greater frequency, and vice versa.

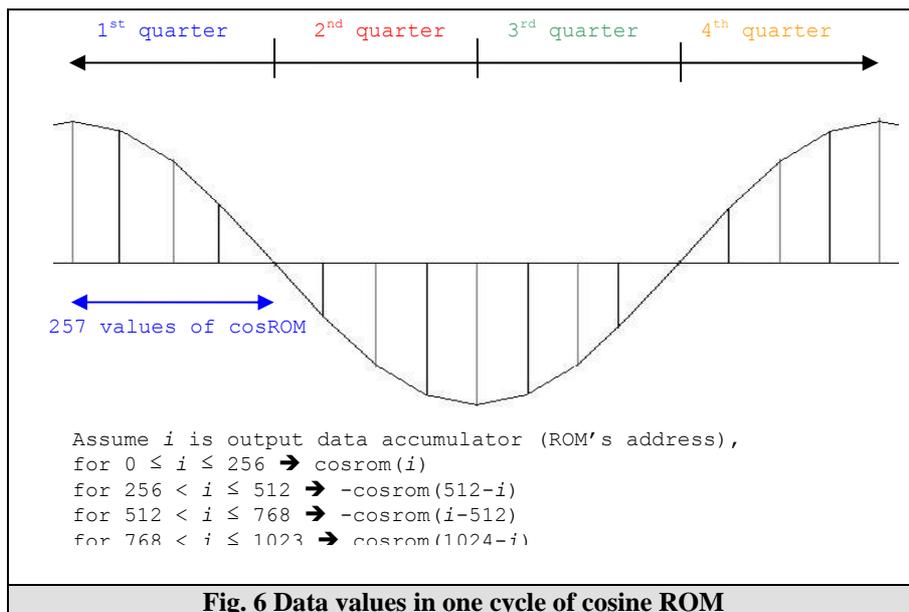

The system is a simple integrator which accumulates the input value and maps it into predefined cosine ROM. All 1024 values were given (*file: cos.txt*) to define one cycle of cosine signal, but we actually don't need to use all of these values. Since one cycle can be divided to four quarter, we only need to define the first quarter with 257 values. The remains quarters are duplicated form the first quarter, where the opposite sign is applied to second and third quarter. Illustration is shown in Fig 6.


Summary of operation:

- input *D2* and *offset* are added, note that signed extension form $\langle 12, -6, t \rangle$ to $\langle 18, 0, u \rangle$.

- the addition result then accumulated by modulo accumulator, then we take 10 most bits as ROM address.
- Address will be mapped to data values in ROM.

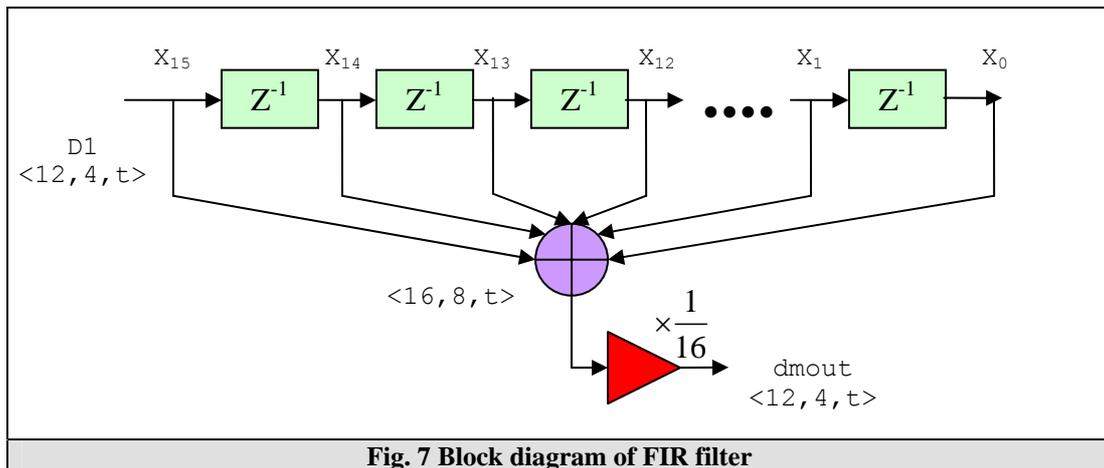2.4 FIR Filter

The last stage of the receiver system is to perform signal shaping. Here we use 16 tap Finite Impulse Response (FIR) filter to perform digital low pass filter. This filter is essentially average filter since its output is equal to the average value of its input over the last n -tap samples, where n is number of tap used [4]. This configuration needs 16 coefficients, but simplification is taken by assuming all of the coefficients are the same, $1/16$. In reality $1/16$ multiply can be implemented by just 4 bit right shift operation. Then no multiplier is required.



3. Functional Explanation

Digital PLL system is composed of three basic parts: (1) Phase Detector (PD), (2) Loop filter, (3) Numerical-controlled oscillator (NCO). The complete block diagram of the All Digital FM receiver circuit is shown in Fig. 8.

With no signal input applied to the system. The NCO control voltage $V_d(n)$ is equal to zero. The NCO operates at a set frequency, f_o (or the equivalent radian frequency, ω_o) which is known as the free running frequency. When an input signal is applied to the system, the phase detector compares the phase and the frequency of the input with the NCO frequency and generates an error voltage $V_e(n)$ that is related to the phase and the frequency difference between the two signals.

frequency changes of the input signal once it is locked, hence it can be act as FM demodulator in receiver system.

Another means of describing the operation of the PLL is to observe that the phase detector is in actuality a multiplier circuit that mixes the input signal with the NCO signal. This mix produces the sum and difference frequencies $(\omega_i \pm \omega_o)$ shown in (3). When the loop is in lock, the NCO duplicates the input frequency so that the difference frequency component $(\omega_i - \omega_o)$ is zero; hence, the output of the phase comparator contains only a DC component. The loop filter removes the sum frequency component $(\omega_i + \omega_o)$ but passes the DC component which is then amplified and fed back to the NCO.

The single most important point to realize when designing with the PLL is that it is a feedback system and, hence, is characterized mathematically by the same equations that apply to other, more conventional feedback control systems [5]. Mathematical model of the all digital PLL system can be derived to analyze the transient and steady state response. The block diagram of the all digital PLL system in z domain (discrete time) and its transformation in s domain (continuous time) is shown in Fig. 9.

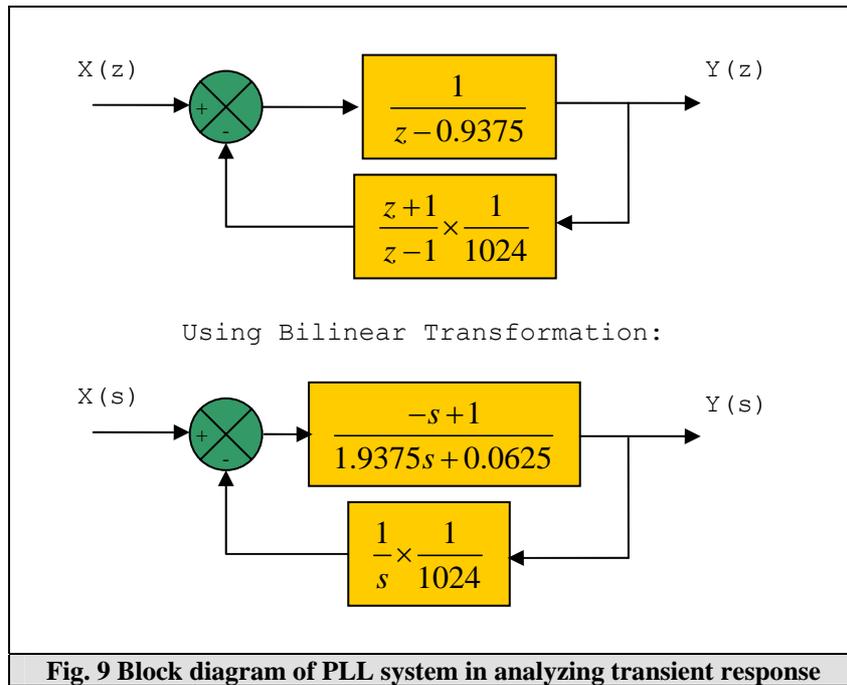


Fig. 9 Block diagram of PLL system in analyzing transient response

Since a physical control system involves energy storage, the output of the system, when subjected to an input, cannot follow the input immediately but exhibits a transient response before a steady state can be reached [3].

The transfer function of the system is

$$\frac{Y(s)}{X(s)} = \frac{-s^2 + s}{1.9375s^2 + 0.06161s + 0.00089} \quad (6)$$

Hence, the PLL system is a second order system. In the test for stability we subjected the system with test signal representing a unit step of frequency at constant phase, this test signal correspond with actual input signal which is a FM modulated signal [5].

Using MATLAB, we can plot unit step response curve for the system as shown in Fig. 10. We see that the system is stable with overshoots at the transient state.

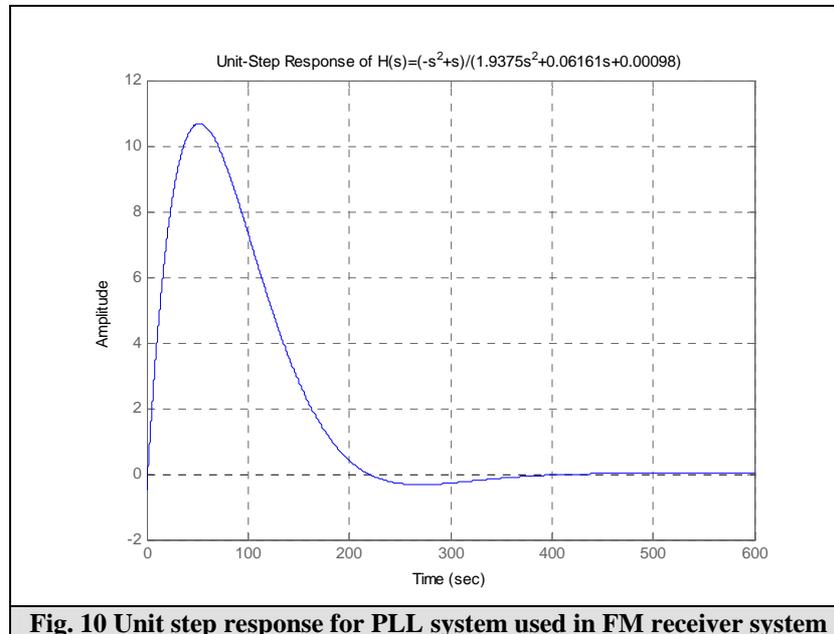


Fig. 10 Unit step response for PLL system used in FM receiver system

4. Critical Path Speed and Circuit Area

Design is synthesized with Xilinx Synthesize Tool (XST), here we use Virtex2 technology with xc2v2000ff896 device and -6 of speed grade.

- Unit delay

The unit speed from synthesizing of 50 input XOR gate (see Appendix for details) give us the result 6.967 ns total delay and 5 levels, then unit delay is $6.967/5 = 1.393$ ns.

- Unit area

The unit area from synthesizing of 50 input XOR gate (see Appendix for details) give us the result 102 total area gate count and utilize 17 cells, then unit area is $102/17 = 6$.

Here is the synthesis result of critical path speed,

```

Timing Summary:
-----
Speed Grade: -6

Minimum period: 8.781ns (Maximum Frequency: 113.889MHz)
Minimum input arrival time before clock: 1.329ns
Maximum output required time after clock: 4.575ns
Maximum combinational path delay: No path found

Timing Detail:
-----
All values displayed in nanoseconds (ns)

-----
Timing constraint: Default period analysis for Clock 'clk'
Delay:          8.781ns (Levels of Logic = 12)
Source:         I2_dtemp1_4 (FF)
Destination:    I2_dout_2 (FF)
Source Clock:   clk rising
Destination Clock: clk rising

Data Path: I2_dtemp1_4 to I2_dout_2

```

| Cell:in->out | fanout | Gate Delay | Net Delay | Logical Name (Net Name) |
|----------------|--------|--|-----------|-----------------------------|
| FDC:C->Q | 12 | 0.449 | 0.688 | I2_dtemp1_4 (I2_dtemp1_4) |
| LUT2_D:I0->LO | 1 | 0.347 | 0.100 | I2_Ker240621 (N65860) |
| LUT4:I3->O | 5 | 0.347 | 0.569 | I2_Ker249151 (I2_N24917) |
| LUT4:I3->O | 2 | 0.347 | 0.518 | I2_Ker2252582 (CHOICE4276) |
| LUT3:I0->O | 1 | 0.347 | 0.000 | I2_Ker2252593_G (N65481) |
| MUXF5:I1->O | 1 | 0.345 | 0.383 | I2_Ker2252593 (CHOICE4278) |
| LUT4:I0->O | 1 | 0.347 | 0.382 | I2_Ker22525105 (CHOICE4279) |
| LUT4_L:I3->LO | 1 | 0.347 | 0.100 | I2_Ker22525154 (CHOICE4291) |
| LUT2:I1->O | 2 | 0.347 | 0.519 | I2_Ker22525164 (I2_N22527) |
| LUT4_L:I3->LO | 1 | 0.347 | 0.100 | I2_Ker22312138 (CHOICE4400) |
| LUT4:I2->O | 2 | 0.347 | 0.518 | I2_Ker22312162 (I2_N22314) |
| LUT4:I3->O | 1 | 0.347 | 0.000 | I2__n0008<2>323_G (N65471) |
| MUXF5:I1->O | | 1 | 0.345 | 0.000 I2__n0008<2>323 |
| (I2__n0008<2>) | | | | |
| FDC:D | | 0.293 | | I2_dout_2 |
| ----- | | | | |
| Total | | 8.781ns (4.902ns logic, 3.878ns route) | | |
| | | (55.8% logic, 44.2% route) | | |

```

-----

```

We conclude that the normalized combinational path delay is $8.781/1.393 = 6.304$ unit delay

While the synthesized result for circuit area is,

```

Design Summary
-----
Number of errors:      0
Number of warnings:   8
Logic Utilization:
  Number of Slice Flip Flops:      446 out of 21,504   2%
  Number of 4 input LUTs:         1,226 out of 21,504   5%
Logic Distribution:
  Number of occupied Slices:       834 out of 10,752   7%
  Number of Slices containing only related logic: 834 out of 834 100%
  Number of Slices containing unrelated logic:    0 out of 834   0%
Total Number 4 input LUTs:        1,248 out of 21,504   5%
  Number used as logic:            1,226
  Number used as a route-thru:     22
  Number of bonded IOBs:           22 out of 624   3%
  IOB Flip Flops:                  20
  Number of GCLKs:                  1 out of 16   6%
Total equivalent gate count for design: 13,835

```

We conclude that the normalized circuit area is $13,835/6 = 2,306$ gates

5. Appealing Point and Originality

The architecture used in this design has been explained in [7]. This architecture is good. We did something different by optimizing phase detector component to achieve smaller circuit area, and we also modify NCO component.

We optimized the multiplication operation used in the phase detector component. We used Booth's algorithm to replace arithmetic multiplier with some adders. This modification reduces the number of gate for this component from 689 gates decrease to 453 gates.

For NCO component, we only need 257x8-bit ROM rather than 1024x8-bit ROM since one cycle of cosine wave can be divided into four quarter as explained before. Although this modification uses smaller size of ROM, we can't avoid using more registers and several comparators, but it's interesting to work with.

We attempted to find another digital PLL architecture like one which was proposed in [8]. We realize that it is also good and easy to build, but it needs high frequency of clock to drive the counters. Finally we try to implement our design into FPGA, and then we need to do real measurement. The result gives us the correct demodulated output wave as expected.

6. HDL Codes

HDL codes for each component, top level design, and the test bench can be observed as follows,

6.1 Multiplier (Phase Detector)

| | |
|---|---|
| <pre> LIBRARY ieee; USE ieee.std_logic_1164.all; USE IEEE.numeric_std.ALL; ENTITY multiplier IS port (CLK : in std logic; RESET : in std logic; input1 : in std_logic_vector(7 downto 0); input2 : in signed(7 downto 0); output : out signed(7 downto 0)); END multiplier ; ARCHITECTURE behavior OF multiplier IS signal out temp : signed(15 downto 0); signal input1 buf : signed(15 downto 0); signal part0,part1,part2,part3,part4, part5,part6,part7 : signed(15 downto 0); begin process (CLK, RESET) begin if (RESET='1') then out temp <= (others => '0');</pre> | <pre> -- Declarations -- input1 as multiplicand <8,0,t> -- input2 as multiplier <8,0,t> -- product <8,0,t> -- output buffer -- multiplicand buffer -- 8 partials product</pre> |
|---|---|

```

output <= (others => '0');
input1_buf <= (others => '0');
part0 <= (others => '0');
part1 <= (others => '0');
part2 <= (others => '0');
part3 <= (others => '0');
part4 <= (others => '0');
part5 <= (others => '0');
part6 <= (others => '0');
part7 <= (others => '0');
elsif rising_edge(CLK) then
    input1_buf <= input1(7)&input1(7)&input1(7)&
                 input1(7)&input1(7)&input1(7)&
                 input1(7)&input1(7)&
                 signed(input1);
    if (input2(0)='1') then
        part0 <= -(input1_buf);
    else
        part0 <= (others => '0');
    end if;

    if (input2(1)='1') then
        if (input2(0)='1') then
            part1 <= (others => '0');
        else
            part1 <= -(input1_buf);
        end if;
    else
        if (input2(0)='1') then
            part1 <= input1_buf;
        else
            part1 <= (others => '0');
        end if;
    end if;

    if (input2(2)='1') then
        if (input2(1)='1') then
            part2 <= (others => '0');
        else
            part2 <= -(input1_buf);
        end if;
    else
        if (input2(1)='1') then
            part2 <= input1_buf;
        else
            part2 <= (others => '0');
        end if;
    end if;

    if (input2(3)='1') then
        if (input2(2)='1') then
            part3 <= (others => '0');
        else
            part3 <= -(input1_buf);
        end if;
    else
        if (input2(2)='1') then
            part3 <= input1_buf;
        else
            part3 <= (others => '0');
        end if;
    end if;

    if (input2(4)='1') then
        if (input2(3)='1') then
            part4 <= (others => '0');
        else
            part4 <= -(input1_buf);
        end if;
    else
        if (input2(3)='1') then
            part4 <= input1_buf;
        else
            part4 <= (others => '0');
        end if;
    end if;
end if;
-- input buffering with sign
-- extension
-- start Booth's algorithm
-- check first bit of multiplier
-- subtract (add 2's complement)

-- no change

-- check second bit of multiplier
-- check previous bit
-- no change

-- subtract (add 2's complement)

-- add

```

| | |
|---|--|
| <pre> if (input2(5)='1') then if (input2(4)='1') then part5 <= (others => '0'); else part5 <= -(input1_buf); end if; else if (input2(4)='1') then part5 <= input1_buf; else part5 <= (others => '0'); end if; end if; if (input2(6)='1') then if (input2(5)='1') then part6 <= (others => '0'); else part6 <= -(input1_buf); end if; else if (input2(5)='1') then part6 <= input1_buf; else part6 <= (others => '0'); end if; end if; if (input2(7)='1') then if (input2(6)='1') then part7 <= (others => '0'); else part7 <= -(input1_buf); end if; else if (input2(6)='1') then part7 <= input1_buf; else part7 <= (others => '0'); end if; end if; out_temp <= part0+(part1(14 downto 0)&'0')+ (part2(13 downto 0)&"00")+ (part3(12 downto 0)&"000")+ (part4(11 downto 0)&"0000")+ (part5(10 downto 0)&"00000")+ (part6(9 downto 0)&"000000")+ (part7(8 downto 0)&"0000000"); output <= out_temp(15 downto 8); end if; end process; END behavior; </pre> | <pre> -- summing partials product -- crop 8 most bits as final product </pre> |
|---|--|

6.2 Loop Filter

| | |
|---|---|
| <pre> LIBRARY ieee; USE ieee.std_logic_1164.all; USE IEEE.numeric_std.ALL; ENTITY loop_filter IS port (CLK : in std_logic; RESET : in std_logic; C : in signed(7 downto 0); D1 : out signed(11 downto 0); D2 : out signed(11 downto 0)); END loop_filter ; </pre> | <pre> -- Declarations -- input <8,0,t> from multiplier -- output <12,4,t> to FIR -- output <12,-6,t> to NCO </pre> |
|---|---|

| | |
|---|--|
| <pre> ARCHITECTURE behavior OF loop filter IS signal E : signed(11 downto 0); signal dtemp : signed(11 downto 0); begin process(CLK, RESET) begin if (RESET='1') then D1 <= (others => '0'); D2 <= (others => '0'); E <= (others => '0'); dtemp <= (others => '0'); elsif rising edge(CLK) then dtemp <= (C(7)&C(7)&C(7)&C(7)&C(7)&C(7)&C(7)&C(7)&C(7)&C(7)&C(7)&C(7)); E <= dtemp(11)&dtemp(11)&dtemp(11)&dtemp(11)&dtemp(11)&dtemp(11)&dtemp(11)&dtemp(11)&dtemp(11)&dtemp(11)&dtemp(11)&dtemp(11); D1 <= dtemp; D2 <= dtemp(11 downto 4)&"0000"; end if; end process; END behavior; </pre> | <pre> -- (Atemp x 1/16) -- output buffer -- 15/16 = (1 - 1/16), -- hence, Atemp x 15/16 = Atemp- (Atemp x 1/16) = Atemp - E -- here we scaled input to get better result -- 1/16 multiply is 4 bit right shift operation -- 1/1024 multiply is 10 bit right shift operation -- D2 = D1 x 1/1024 -- note that to get D2, D1 must be changed to 18 bit then do the 10 bit shift right operation and then change it to <12,-6,t> format. </pre> |
|---|--|

6.3 Numerical Controlled Oscillator (NCO)

| | |
|--|---|
| <pre> LIBRARY ieee; USE ieee.std_logic_1164.all; USE IEEE.numeric_std.ALL; ENTITY nco IS port(clk : in std_logic; reset : in std_logic; din : in signed(11 downto 0); dout : out signed(7 downto 0)); END nco ; ARCHITECTURE behavior OF nco IS type vectype is array (0 to 256) of signed(7 downto 0); constant cosrom : vectype := (0 => "01111111", 1 => "01111111", 2 => "01111111", 3 => "01111111", 4 => "01111111", 5 => "01111111", 6 => "01111111", 7 => "01111111", 8 => "01111111", 9 => "01111111", 10 => "01111111", 11 => "01111111", 12 => "01111111", 13 => "01111111", 14 => "01111111", 15 => "01111111", 16 => "01111111", 17 => "01111111", 18 => "01111111", 19 => "01111111", 20 => "01111111", 21 => "01111111", 22 => "01111111", 23 => "01111111", 24 => "01111111", </pre> | <pre> -- Declarations -- input <12,-6,t> from loop filter -- output data from cosine ROM <8,0,t> -- using first quarter data (257) values of file: cos.txt -- cosine ROM </pre> |
|--|---|

| | |
|--------------------|--|
| 25 => "01111110", | |
| 26 => "01111110", | |
| 27 => "01111110", | |
| 28 => "01111110", | |
| 29 => "01111110", | |
| 30 => "01111110", | |
| 31 => "01111110", | |
| 32 => "01111110", | |
| 33 => "01111101", | |
| 34 => "01111101", | |
| 35 => "01111101", | |
| 36 => "01111101", | |
| 37 => "01111101", | |
| 38 => "01111101", | |
| 39 => "01111100", | |
| 40 => "01111100", | |
| 41 => "01111100", | |
| 42 => "01111100", | |
| 43 => "01111100", | |
| 44 => "01111011", | |
| 45 => "01111011", | |
| 46 => "01111011", | |
| 47 => "01111011", | |
| 48 => "01111010", | |
| 49 => "01111010", | |
| 50 => "01111010", | |
| 51 => "01111010", | |
| 52 => "01111010", | |
| 53 => "01111001", | |
| 54 => "01111001", | |
| 55 => "01111001", | |
| 56 => "01111001", | |
| 57 => "01111000", | |
| 58 => "01111000", | |
| 59 => "01111000", | |
| 60 => "01110111", | |
| 61 => "01110111", | |
| 62 => "01110111", | |
| 63 => "01110111", | |
| 64 => "01110110", | |
| 65 => "01110110", | |
| 66 => "01110110", | |
| 67 => "01110101", | |
| 68 => "01110101", | |
| 69 => "01110101", | |
| 70 => "01110100", | |
| 71 => "01110100", | |
| 72 => "01110100", | |
| 73 => "01110011", | |
| 74 => "01110011", | |
| 75 => "01110011", | |
| 76 => "01110010", | |
| 77 => "01110010", | |
| 78 => "01110010", | |
| 79 => "01110001", | |
| 80 => "01110001", | |
| 81 => "01110001", | |
| 82 => "01110000", | |
| 83 => "01110000", | |
| 84 => "01101111", | |
| 85 => "01101111", | |
| 86 => "01101111", | |
| 87 => "01101110", | |
| 88 => "01101110", | |
| 89 => "01101101", | |
| 90 => "01101101", | |
| 91 => "01101101", | |
| 92 => "01101100", | |
| 93 => "01101100", | |
| 94 => "01101011", | |
| 95 => "01101011", | |
| 96 => "01101010", | |
| 97 => "01101010", | |
| 98 => "01101010", | |
| 99 => "01101001", | |
| 100 => "01101001", | |

| | | |
|--------------------|--|--|
| 101 => "01101000", | | |
| 102 => "01101000", | | |
| 103 => "01100111", | | |
| 104 => "01100111", | | |
| 105 => "01100110", | | |
| 106 => "01100110", | | |
| 107 => "01100101", | | |
| 108 => "01100101", | | |
| 109 => "01100100", | | |
| 110 => "01100100", | | |
| 111 => "01100011", | | |
| 112 => "01100011", | | |
| 113 => "01100010", | | |
| 114 => "01100010", | | |
| 115 => "01100001", | | |
| 116 => "01100001", | | |
| 117 => "01100000", | | |
| 118 => "01100000", | | |
| 119 => "01011111", | | |
| 120 => "01011111", | | |
| 121 => "01011110", | | |
| 122 => "01011110", | | |
| 123 => "01011101", | | |
| 124 => "01011101", | | |
| 125 => "01011100", | | |
| 126 => "01011100", | | |
| 127 => "01011011", | | |
| 128 => "01011011", | | |
| 129 => "01011010", | | |
| 130 => "01011001", | | |
| 131 => "01011001", | | |
| 132 => "01011000", | | |
| 133 => "01011000", | | |
| 134 => "01010111", | | |
| 135 => "01010111", | | |
| 136 => "01010110", | | |
| 137 => "01010101", | | |
| 138 => "01010101", | | |
| 139 => "01010100", | | |
| 140 => "01010100", | | |
| 141 => "01010011", | | |
| 142 => "01010010", | | |
| 143 => "01010010", | | |
| 144 => "01010001", | | |
| 145 => "01010001", | | |
| 146 => "01010000", | | |
| 147 => "01001111", | | |
| 148 => "01001111", | | |
| 149 => "01001110", | | |
| 150 => "01001110", | | |
| 151 => "01001101", | | |
| 152 => "01001100", | | |
| 153 => "01001100", | | |
| 154 => "01001011", | | |
| 155 => "01001010", | | |
| 156 => "01001010", | | |
| 157 => "01001001", | | |
| 158 => "01001000", | | |
| 159 => "01001000", | | |
| 160 => "01000111", | | |
| 161 => "01000111", | | |
| 162 => "01000110", | | |
| 163 => "01000101", | | |
| 164 => "01000101", | | |
| 165 => "01000100", | | |
| 166 => "01000011", | | |
| 167 => "01000011", | | |
| 168 => "01000010", | | |
| 169 => "01000001", | | |
| 170 => "01000001", | | |
| 171 => "01000000", | | |
| 172 => "00111111", | | |
| 173 => "00111110", | | |
| 174 => "00111110", | | |
| 175 => "00111101", | | |
| 176 => "00111100", | | |

| | | |
|---------------------|--|--|
| 177 => "001111100", | | |
| 178 => "001111011", | | |
| 179 => "001111010", | | |
| 180 => "001111010", | | |
| 181 => "001111001", | | |
| 182 => "001111000", | | |
| 183 => "001111000", | | |
| 184 => "001110111", | | |
| 185 => "001110110", | | |
| 186 => "001110101", | | |
| 187 => "001110101", | | |
| 188 => "001110100", | | |
| 189 => "001110011", | | |
| 190 => "001110011", | | |
| 191 => "001110010", | | |
| 192 => "001110001", | | |
| 193 => "001110000", | | |
| 194 => "001110000", | | |
| 195 => "001011111", | | |
| 196 => "001011110", | | |
| 197 => "001011101", | | |
| 198 => "001011101", | | |
| 199 => "001011100", | | |
| 200 => "001010111", | | |
| 201 => "001010101", | | |
| 202 => "001010101", | | |
| 203 => "001010011", | | |
| 204 => "001010000", | | |
| 205 => "001001111", | | |
| 206 => "001001111", | | |
| 207 => "001001110", | | |
| 208 => "001001011", | | |
| 209 => "001001000", | | |
| 210 => "001001000", | | |
| 211 => "001000111", | | |
| 212 => "001000100", | | |
| 213 => "001000011", | | |
| 214 => "001000011", | | |
| 215 => "001000000", | | |
| 216 => "000111111", | | |
| 217 => "000111110", | | |
| 218 => "000111110", | | |
| 219 => "000111101", | | |
| 220 => "000111100", | | |
| 221 => "000111011", | | |
| 222 => "000111011", | | |
| 223 => "000111010", | | |
| 224 => "000111001", | | |
| 225 => "000111000", | | |
| 226 => "000111000", | | |
| 227 => "000101111", | | |
| 228 => "000101110", | | |
| 229 => "000101101", | | |
| 230 => "000101100", | | |
| 231 => "000101100", | | |
| 232 => "000100111", | | |
| 233 => "000100101", | | |
| 234 => "000100011", | | |
| 235 => "000100011", | | |
| 236 => "000100000", | | |
| 237 => "000011111", | | |
| 238 => "000011110", | | |
| 239 => "000011101", | | |
| 240 => "000011101", | | |
| 241 => "000011100", | | |
| 242 => "000010111", | | |
| 243 => "000010110", | | |
| 244 => "000010110", | | |
| 245 => "000010011", | | |
| 246 => "000010000", | | |
| 247 => "000001111", | | |
| 248 => "000001110", | | |
| 249 => "000001110", | | |
| 250 => "000001011", | | |
| 251 => "000001000", | | |
| 252 => "000000111", | | |

| | |
|--|---|
| <pre> 253 => "00000010", 254 => "00000010", 255 => "00000001", 256 => "00000000"); signal dtemp : unsigned(17 downto 0); signal dtempl : integer; signal din_buf : signed(17 downto 0); constant offset : unsigned(17 downto 0) := "000100000000000000"; begin process(CLK, RESET) begin if (RESET='1') then dout <= (others => '0'); din_buf <= (others => '0'); dtemp <= (others => '0'); dtempl <= 0; elsif rising edge(CLK) then din_buf <= din(11) & din(11) & din(11) & din(11) & din(11) & din(11) & din; dtemp <= dtemp + unsigned(din_buf) + offset; dtempl <= to_integer(dtemp(17 downto 8)); if (dtempl >= 0) and (dtempl < 257) then dout <= cosrom(dtempl); elsif (dtempl >= 257) and (dtempl < 513) then dout <= -cosrom(512-dtempl); elsif (dtempl >= 513) and (dtempl < 769) then dout <= -cosrom(dtempl-512); else dout <= cosrom(1024-dtempl); end if; end if; end process; END behavior; </pre> | <pre> -- modulo accumulator buffer -- offset = 1/16 <18,0,u> -- sign extension -- accumulator -- mapping input to data values Assume i is output data accumulator, for 0 ≤ i ≤ 256 → cosrom(i) for 256 < i ≤ 512 → -cosrom(512-i) for 512 < i ≤ 768 → -cosrom(i-512) for 768 < i ≤ 1023 → cosrom(1024- i) </pre> |
|--|---|

6.4 FIR Filter

| | |
|---|---|
| <pre> LIBRARY ieee; USE IEEE.std_logic_1164.all; USE IEEE.numeric_std.ALL; entity FIR is port(clock : in std_logic; reset : in std_logic; data_in : in signed(11 downto 0); data_out : out std_logic_vector(11 downto 0)); end FIR; architecture behavior of FIR is signal d0,d1,d2,d3,d4,d5,d6,d7,d8,d9,d10, d11,d12,d13,d14,d15 : signed(15 downto 0); signal sum : signed(15 downto 0); begin process(clock,reset) begin if (reset = '1') then d0 <= (others => '0'); d1 <= (others => '0'); d2 <= (others => '0'); d3 <= (others => '0'); d4 <= (others => '0'); d5 <= (others => '0'); d6 <= (others => '0'); d7 <= (others => '0'); d8 <= (others => '0'); d9 <= (others => '0'); d10 <= (others => '0'); d11 <= (others => '0'); </pre> | <pre> -- declaration -- input 12 bit -- ouput 12 bit -- 16 tap FIR -- buffer </pre> |
|---|---|

| | |
|--|--|
| <pre> d12 <= (others => '0'); d13 <= (others => '0'); d14 <= (others => '0'); d15 <= (others => '0'); sum <= (others => '0'); data out <= (others => '0'); ELSIF rising edge(clock) THEN d0 <= data in(11)&data in(11)& data in(11)&data in(11)&data in; d1 <= d0; d2 <= d1; d3 <= d2; d4 <= d3; d5 <= d4; d6 <= d5; d7 <= d6; d8 <= d7; d9 <= d8; d10 <= d9; d11 <= d10; d12 <= d11; d13 <= d12; d14 <= d13; d15 <= d14; sum <= (d0+d1+d2+d3+d4+d5+d6+d7+d8+d9+ d10+d11+d12+d13+d14+d15) srl 4; data_out <= std_logic_vector(sum(11 downto 0)); end if; end process; end behavior; </pre> | <pre> -- 1/16 multiply is 4 bit right shift operation </pre> |
|--|--|

6.5 Circuit (top level design)

| | |
|--|---|
| <pre> LIBRARY ieee; USE ieee.std_logic_1164.all; USE IEEE.numeric_std.ALL; ENTITY circuit IS PORT(clk : IN std_logic; reset : IN std_logic; fmin : IN std_logic_vector(7 downto 0); dmout : OUT std_logic_vector (11 DOWNTO 0)); END circuit ; ARCHITECTURE behavior OF circuit IS SIGNAL d1 : signed(11 DOWNTO 0); SIGNAL d2 : signed(11 DOWNTO 0); SIGNAL dout : signed(7 DOWNTO 0); SIGNAL output : signed(7 DOWNTO 0); COMPONENT multiplier PORT (clk : IN std_logic ; reset : IN std_logic ; input1 : IN std_logic_vector (7 DOWNTO 0); input2 : IN signed (7 DOWNTO 0); output : OUT signed (7 DOWNTO 0)); END COMPONENT; COMPONENT fir PORT (clock : IN std_logic ; reset : IN std_logic ; data in : IN signed (11 DOWNTO 0); data out : OUT std_logic_vector (11 DOWNTO 0)); END COMPONENT; COMPONENT loop_filter PORT (clk : IN std_logic ; </pre> | <pre> -- declaration -- modulated data input -- demodulated data output -- Architecture declarations -- Internal signal declarations -- Component Declarations </pre> |
|--|---|

| | |
|--|---|
| <pre> reset : IN std logic ; c : IN signed (7 DOWNT0 0); d1 : OUT signed (11 DOWNT0 0); d2 : OUT signed (11 DOWNT0 0)); END COMPONENT; COMPONENT nco PORT (clk : IN std logic ; reset : IN std logic ; din : IN signed (11 DOWNT0 0); dout : OUT signed (7 DOWNT0 0)); END COMPONENT; BEGIN I1 : multiplier PORT MAP (clk => clk, reset => reset, input1 => fmin, input2 => dout, output => output); I4 : fir PORT MAP (clock => clk, reset => reset, data_in => d1, data out => dmout); I3 : loop filter PORT MAP (clk => clk, reset => reset, c => output, d1 => d1, d2 => d2); I2 : nco PORT MAP (clk => clk, reset => reset, din => d2, dout => dout); END behavior; </pre> | <pre> -- Instance port mappings. </pre> |
|--|---|

6.6 Test Bench

| | |
|--|---|
| <pre> LIBRARY ieee; USE ieee.std_logic_1164.ALL; USE IEEE.numeric_std.ALL; USE std.textio.ALL; ENTITY circuit tb IS END circuit tb; ARCHITECTURE behavior OF circuit_tb IS file_vectors: text open read mode is "fm.txt"; COMPONENT circuit PORT(clk : IN std_logic; reset : IN std_logic; fmin : IN std_logic_vector(7 downto 0); dmout : OUT std_logic_vector(11 downto 0)); END COMPONENT; </pre> | <pre> -- input read from given file: "fm.txt" for square modulated signal and "fmtri.txt" for triangular modulated signal -- Component Declarations </pre> |
|--|---|

| | |
|--|---|
| <pre> SIGNAL clk : std logic := '0' ; SIGNAL reset : std logic := '1'; SIGNAL fmin : std logic vector(7 downto 0); SIGNAL dmout : std logic_vector(11 downto 0); constant clkperiod : time := 62.5 ns; BEGIN uut: circuit PORT MAP(clk => clk, reset => reset, fmin => fmin, dmout => dmout); RESET_GEN: process begin LOOP1: for N in 0 to 3 loop wait until falling edge(CLK); end loop LOOP1; RESET <= '0' ; end process RESET_GEN; clk <= not clk after clkperiod / 2; process variable vectorline : line; variable fmin_var : bit_vector(7 downto 0); begin while not endfile(vectors) loop if (reset = '1') then fmin <= (others => '0'); else readline(vectors, vectorline); read(vectorline, fmin_var); fmin <= to_stdlogicvector(fmin_var); end if; wait for clkperiod; end loop; end process; END;</pre> | <pre> -- Internal signal declarations -- system clock frequency = 16 MHz -- Instance port mappings. -- reset signal generator -- clock signal generator -- read file vector operation.</pre> |
|--|---|

7. Simulation Waveform

Fig. 11 shows the simulation waveform for all digital FM receiver circuit subjected to square wave modulated data, while Fig. 12 shows the simulation waveform for All Digital FM Receiver circuit subjected to triangular wave modulated data. The first row shows the FM modulated waveform according to the sending data. The second row is NCO output and the third row is phase detector (multiplier) output. The fourth row and the fifth row are the accumulator output and the demodulated output, respectively. At the initial simulation phase, the demodulated output overshoots since the phase synchronization is in convergence phase and then system is stable.

From Fig. 11 and Fig. 12, designed FM receiver circuit successfully demodulates input signal back to the original signal.

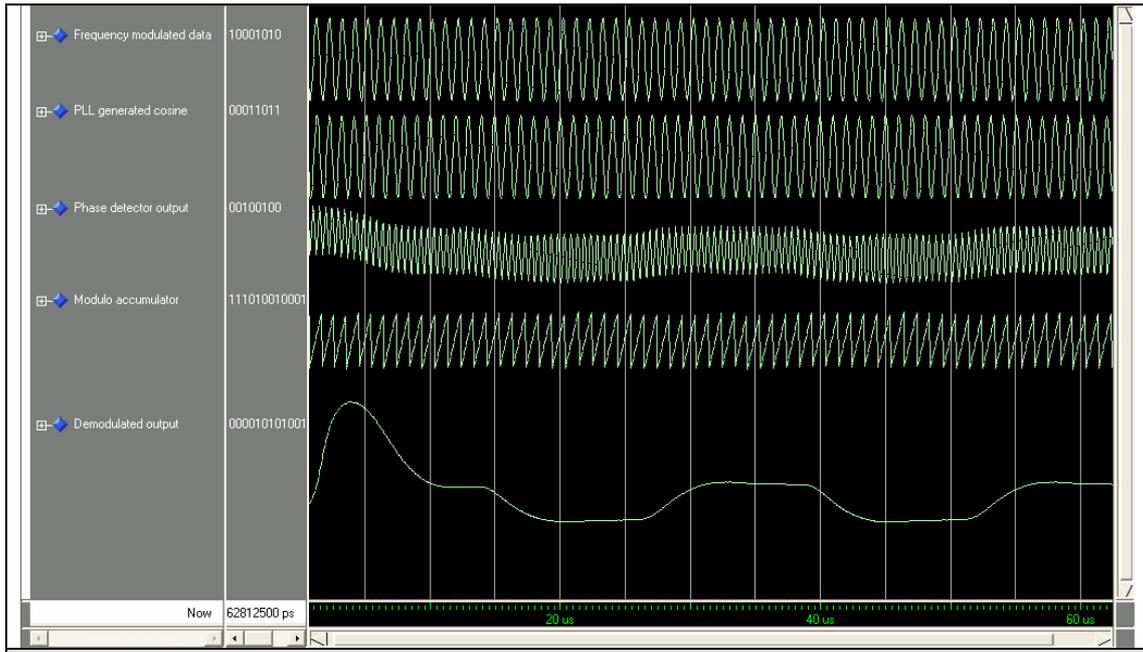


Fig. 11 Simulation waveform of the circuit, subjected to square wave modulated input signal

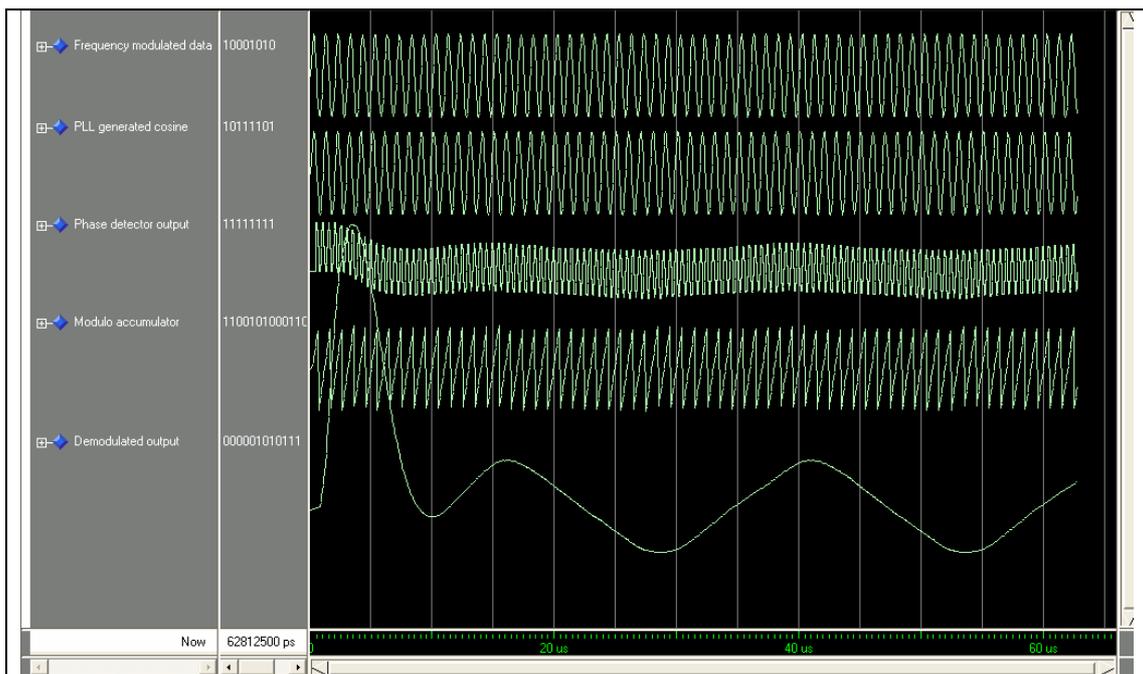


Fig. 12 Simulation waveform of the circuit, subjected to triangular wave modulated input signal

8. FPGA Implementation

We implement the all digital FM receiver circuit designed into FPGA. Here we are using Virtex2 device from Xilinx with XC2V2000 technology and ff896 package. The chip graphic is shown in Fig.13

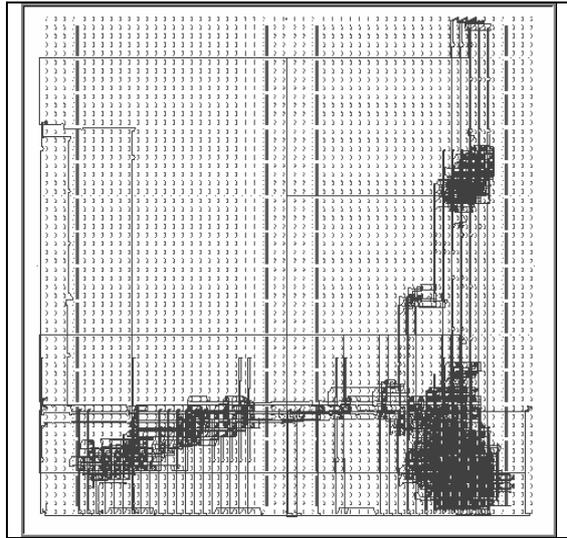


Fig. 13 Chip graphic for the design

ChipScope Pro 6.3i provides an integrated logic analyzer used to capture data in the designed circuit. After design is downloaded to FPGA board, ChipScope Pro will trigger input data and capture the output data via parallel cable in JTAG Boundary Scan mode as shown in Fig. 14. Captured data is in the listing form of 12-bit binary number as shown in Fig. 15. We can adjust how many samples needed to be captured; here we captured 1024 samples output data, then we plot it by ModelSim to obtain the actual demodulated signal view as shown in Fig.16

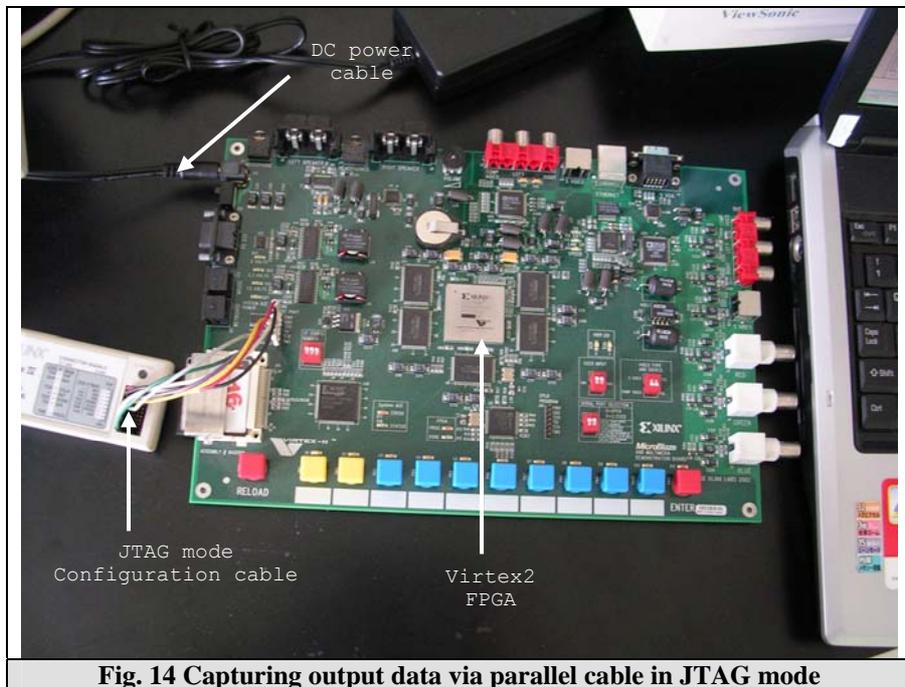


Fig. 14 Capturing output data via parallel cable in JTAG mode

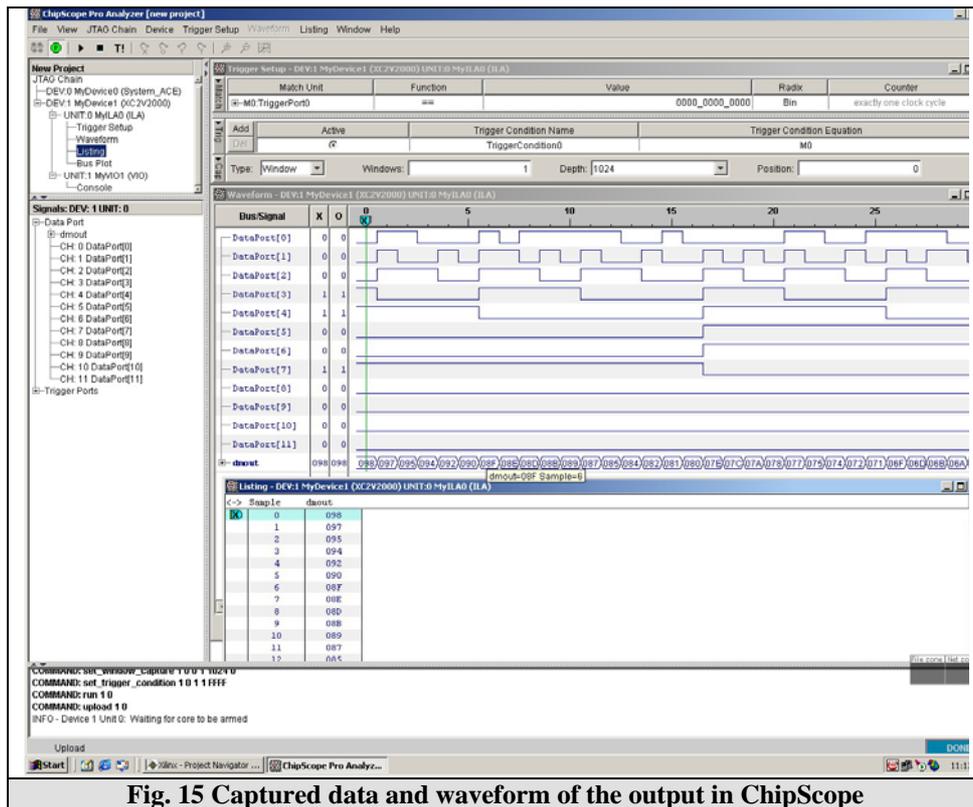


Fig. 15 Captured data and waveform of the output in ChipScope

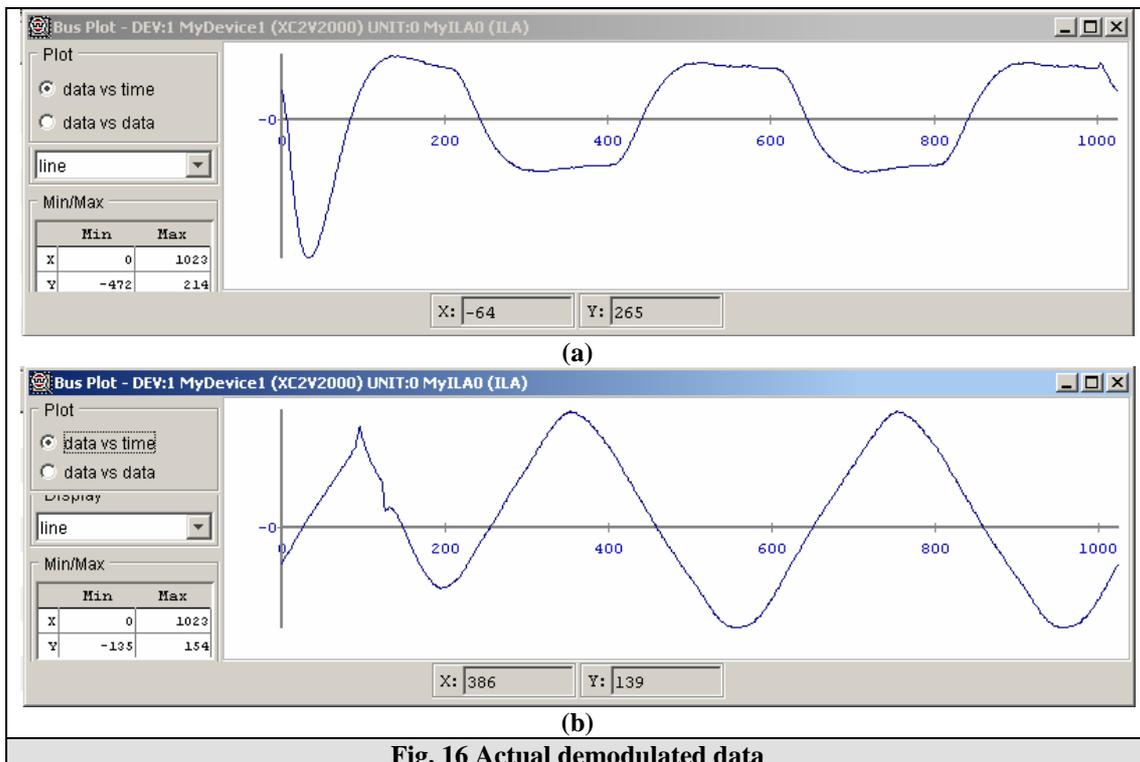


Fig. 16 Actual demodulated data

9. Closing

VHDL and FPGA are always attracting us in our VLSI System Design class. We are enthusiast in joining this program. This subject of study is new for us as beginners, now we can learn basic principle of digital FM receiver and get the opportunity to make our design, we enjoy it. We've found this a great subject to work in because we've gained knowledge about the state of the VLSI Design, its different sectors and the links that exist within it and between other global electronics study.

誰にもまちがいはある、だからエンピツにも消しゴムがついている。

Reference:

- [1] “*Modeling PLL*,” in Integrated Circuits Application Note AN178 Philips Semiconductors, 1988.
- [2] Douglas J. Smith, “*HDL Chip Design*,” Doone Publication, 1996
- [3] John G. Proakis, Dimitri G. Manolakis, “*Digital Signal Processing*,” Prentice Hall, 1996.
- [4] Katsuhiko Ogata, “*Modern Control Engineering*,” Prentice Hall, 2002.
- [5] Naresh K. Sinha, “*Linear Systems*,” John Wiley and Sons. Inc, 1991.
- [6] P.E. Allen, “*All Digital Phase Locked Loop*,” in Lecture Note CMOS Phase Locked Loops, 2003.
- [7] Roland E. Best, “*Phase Locked Loop, Theory, Design, and Applications*,” McGraw – Hill, 2003.
- [8] Website : http://bw-www.ie.u-ryukyu.ac.jp/~wada/design05/spec_e.html

Appendix:

Synthesis result of 50 input XOR gate for computing unit delay

Timing Detail:

All values displayed in nanoseconds (ns)

Timing constraint: Default path analysis

Delay: 6.967ns (Levels of Logic = 5)

Source: A<10> (PAD)

Destination: Y (PAD)

Data Path: A<10> to Y

| Cell:in->out | fanout | Gate Delay | Net Delay | Logical Name (Net Name) |
|--------------|--------|------------|--------------------------------|--------------------------------------|
| IBUF:I->O | 1 | 0.653 | 0.383 | A_10_IBUF (A_10_IBUF) |
| LUT4:I0->O | 1 | 0.347 | 0.383 | Mxor_Y_inst_lut4_01 (Mxor_Y__net0) |
| LUT4:I0->O | 1 | 0.347 | 0.383 | Mxor_Y_inst_lut4_121 (Mxor_Y__net14) |
| LUT4:I0->O | 1 | 0.347 | 0.383 | Mxor_Y_inst_lut4_151 (Y_OBUF) |
| OBUF:I->O | | 3.743 | | Y_OBUF (Y) |
| ----- | | | | |
| Total | | 6.967ns | (5.437ns logic, 1.530ns route) | (78.0% logic, 22.0% route) |

Synthesis result of 50 input XOR gate for computing unit area

Design Summary

Number of errors: 0

Number of warnings: 0

Logic Utilization:

Number of 4 input LUTs: 17 out of 21,504 1%

Logic Distribution:

Number of occupied Slices: 13 out of 10,752 1%

Number of Slices containing only related logic: 13 out of 13 100%

Number of Slices containing unrelated logic: 0 out of 13 0%

*See NOTES below for an explanation of the effects of unrelated logic

Total Number 4 input LUTs: 17 out of 21,504 1%

Number of bonded IOBs: 51 out of 624 8%

Total equivalent gate count for design: 102

Additional JTAG gate count for IOBs: 2,448

Peak Memory Usage: 100 MB